
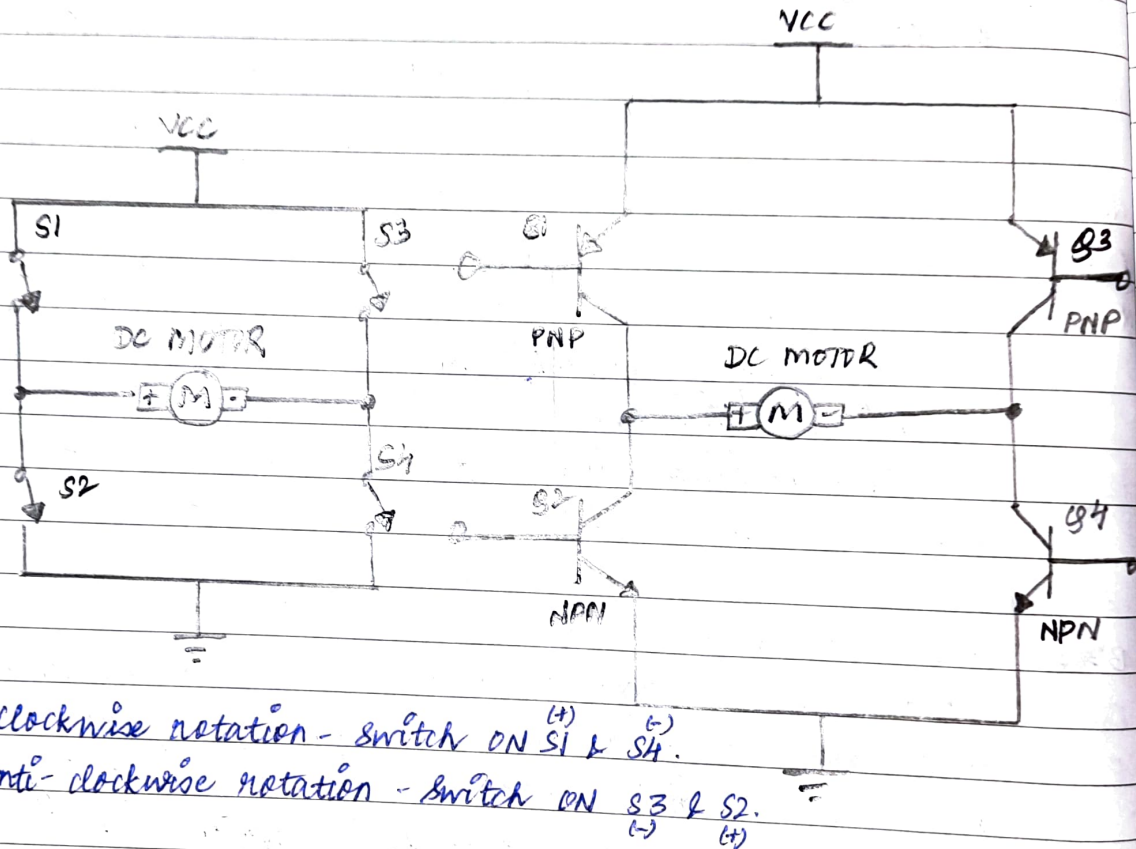


LECTURE 31- DC MOTOR CONTROL

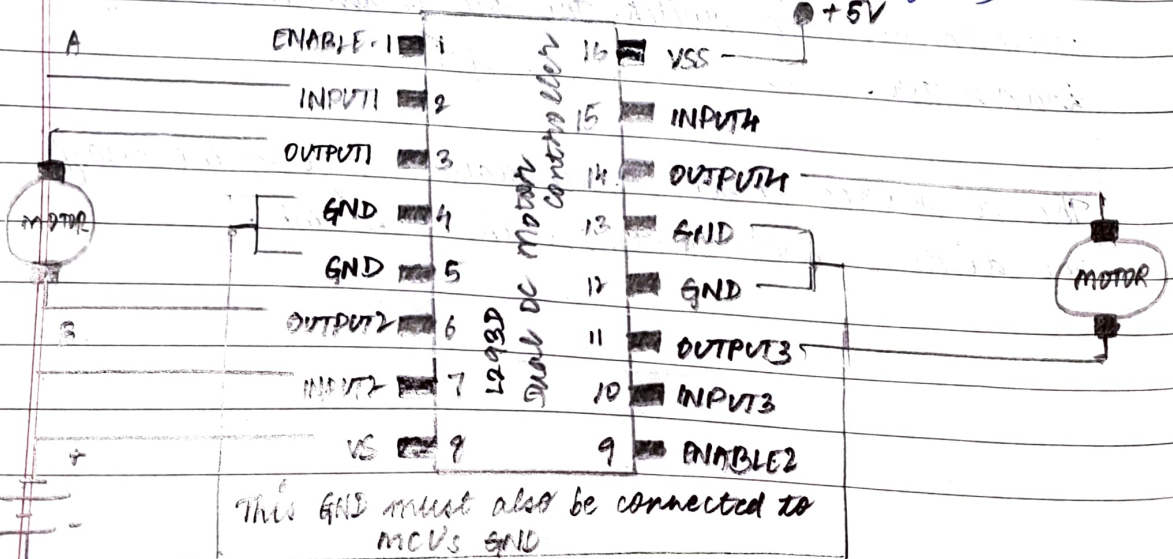In the earlier lecture, we had controlled the motor using a relay. Here, we'll control the direction of the DC motor, using H Bridge



clockwise rotation - Q1 (Logic 0) & Q4 (Logic 1).  
 Anti-clockwise rotation - Q3 (Logic 0) & Q2 (Logic 1).



There are <sup>two</sup> H bridges which can be used to control <sup>two</sup> DC motors. All the transistors mentioned earlier are embedded in this IC. This can control the direction of two DC motors.

Pin Number 16 (VSS) acts as VCC to the IC. This is programmed as 0V since the IC works on 5V voltage supply, not 3.3V as in the earlier lectures. Four grounds are present in this IC, all of which are shorted.

Pin Number 8 (VS) is the <sup>source</sup> voltage that has to be applied to the motor. Since we are using 5V motor, we are equating VS to 5V. Input 1 and 2 are used to give input to motor 1. Similarly, input 3 and 4 are used to give input to motor 2.



The first motor is connected across output 1 and 2. Similarly, the second motor is connected across output 3 and 4. To rotate the first motor in clockwise direction, we need to give 1 and 0 as input to input 1 and 2 respectively. To rotate it in the anticlockwise direction, we need to give 0 and 1 as input to input 1 and 2 respectively.

To rotate the second motor in clockwise direction, we need to give 1 and 0 as input 4 and 3 respectively. To rotate it in the anticlockwise direction, we need to give 0 and 1 as input to input 4 and 3 respectively.




LECTURE 32 - STEPPER MOTOR CONTROL\* STEP ANGLE:Step Angle =  $45^\circ$ 

Number of steps required to complete a rotation = 8

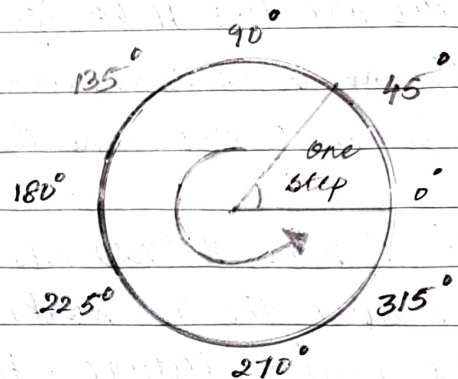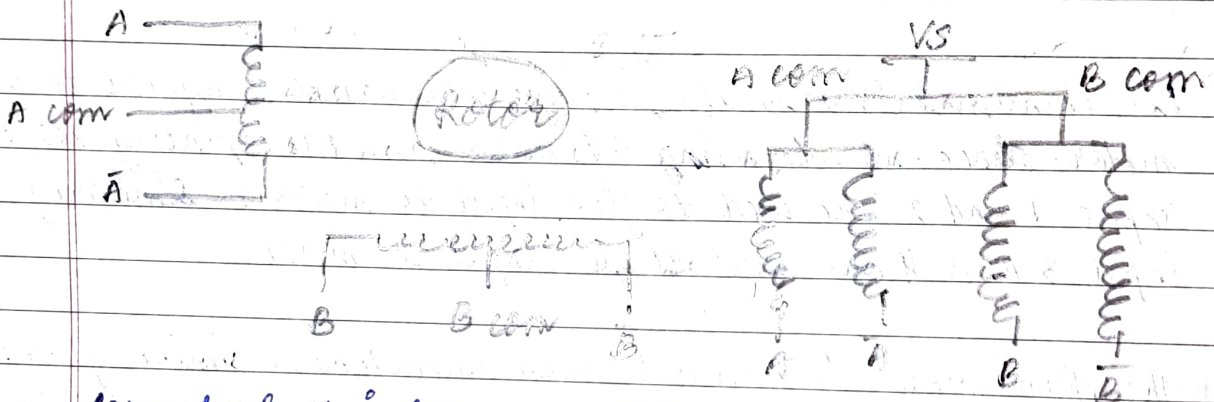\* UNIPOLAR STEPPER:

Conceptual unipolar stepper motor diagram


This popular configuration is used where, motor supply is connected to centres of both winding and ground to each winding end. is controlled through motor driver circuit and microcontroller.

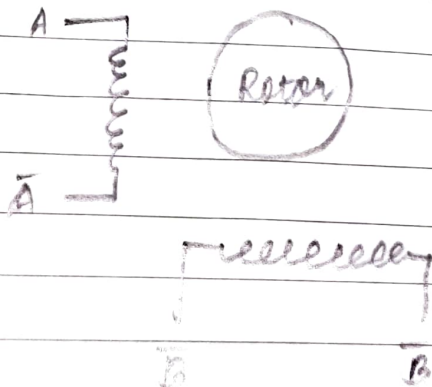\* BIPOLAR STEPPER:

## Conceptual Bipolar Stepper Motor Diagram

This configuration requires control of current direction flow through each winding to control alteration of magnetic poles on winding required to attract and repel respective rotor poles.

### \* PERMANENT MAGNET STEPPER:

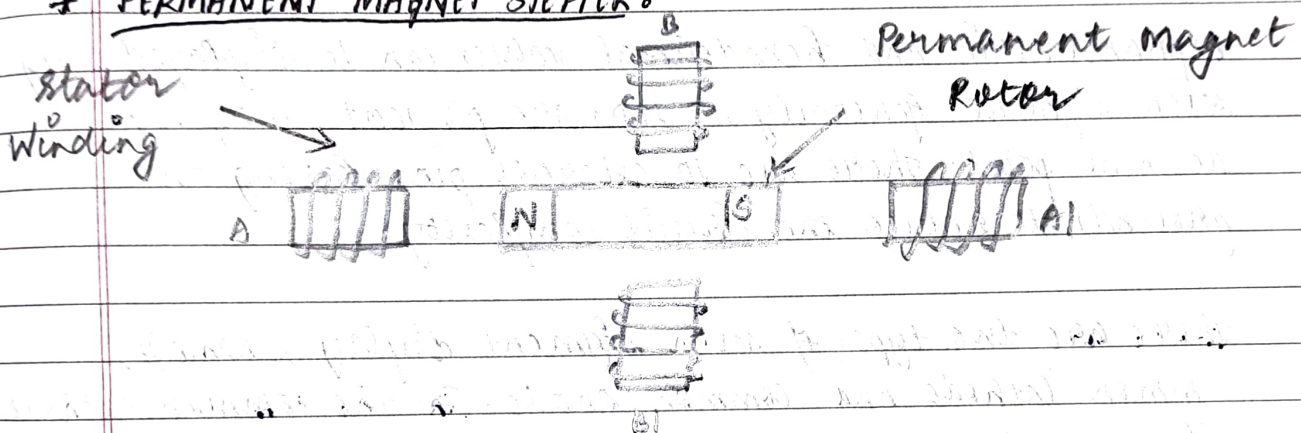

Stepper motor is a brushless DC motor that divides the full rotation angle of  $360^\circ$  into number of equal steps. The motor is rotated by applying a certain sequence of control signals. The speed of rotation can be changed by changing the rate at which the control signals are applied.

Various stepper motors with different step angles and torque ratings are available in the market. Microcontroller can be used to apply different control signals to the motor to make it rotate according to the need of the application.

To find winding coils and their centre tap leads, measure resistance in between the leads. From centre leads we will get half the resistance value as compared to the resistance between winding ends.